
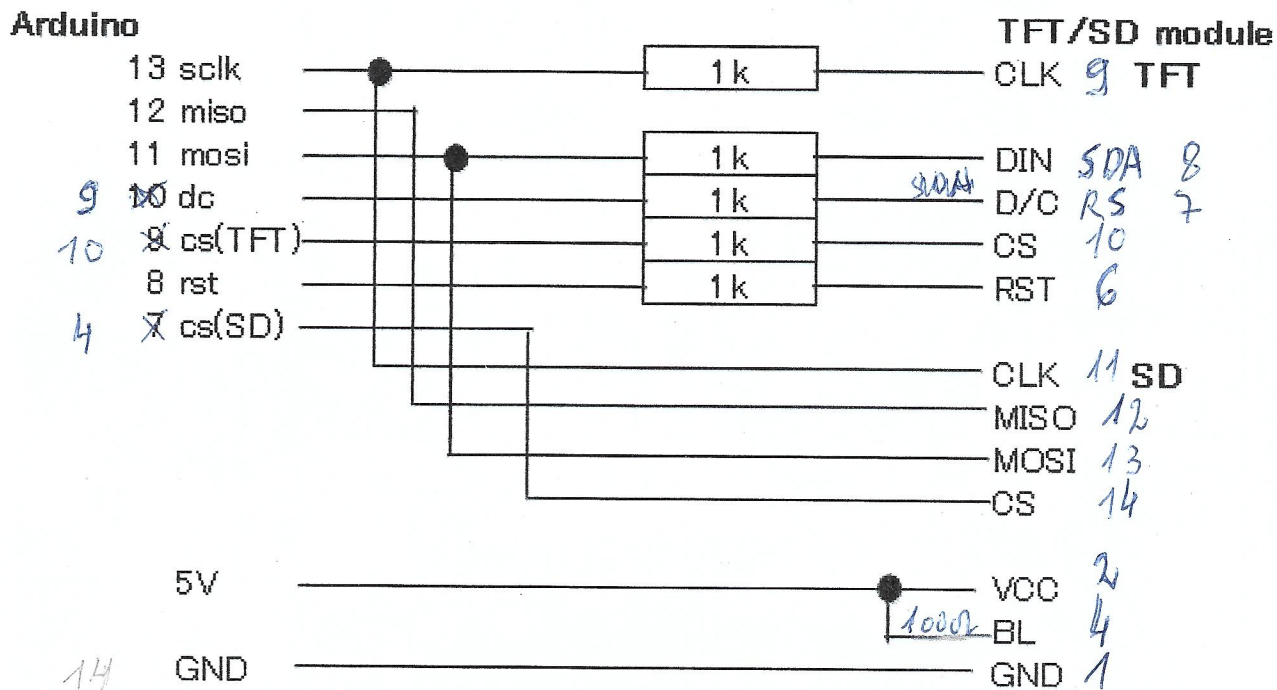


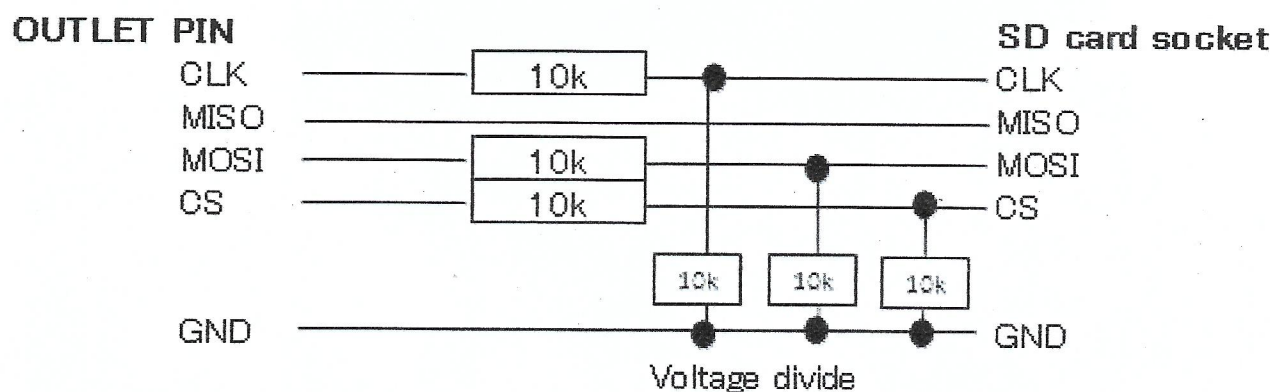
## Arduino to TFT/SD module shield circuit



## TFT/SD module



Pin 3, 5, 6 Pin Arduino

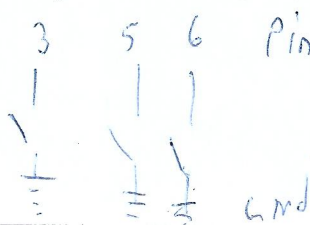

moisture sensor  $\gamma_L = 69$



Arduino

A0 → ~~Analog~~ analog pin


D0 → digital pin

GND → GND

VCC → 5V

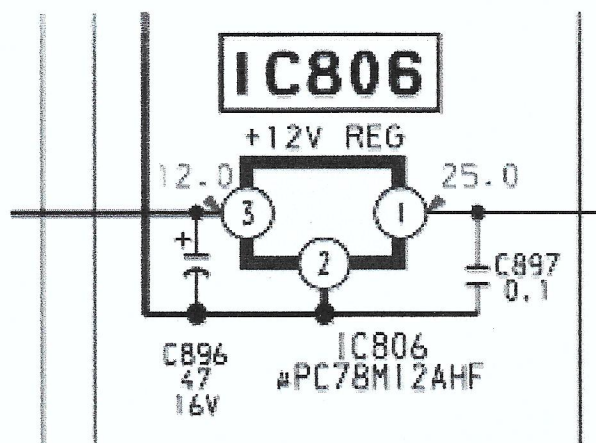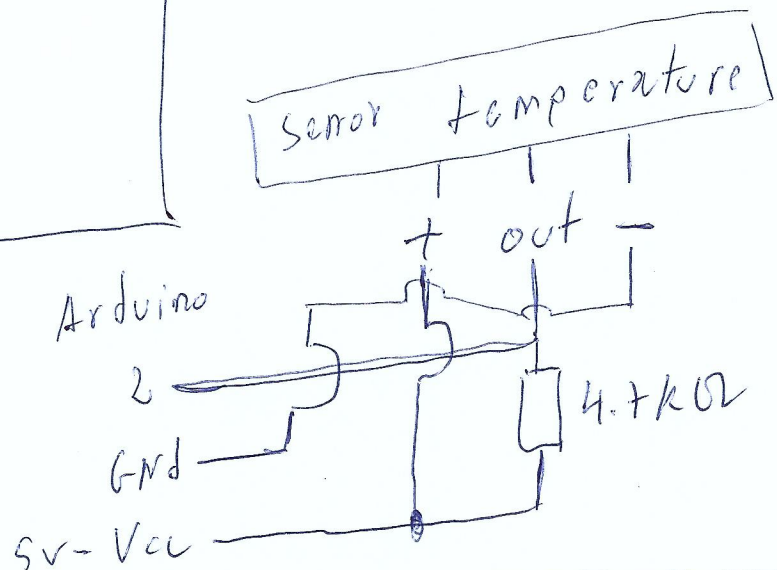

DS18B20  
temperature  
sensor  
+ out =

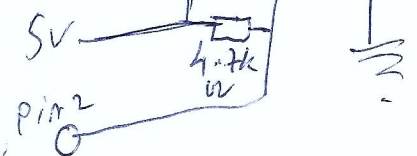

Light Intensity sensor - 5528


Arduino

~~A0~~ A1 SIG

VCC VCC 5V

GND GND
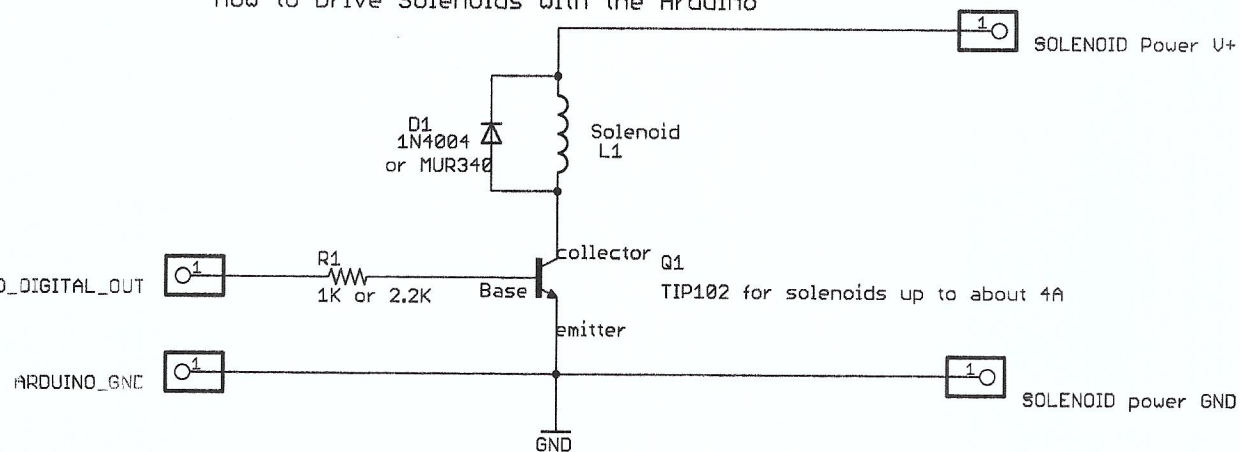
# How to Drive Solenoids with the Arduino



## Notes:

- you will most likely need a heat sink on the transistor.
- This diagram is for DC solenoids rated up to about 24W: i.e. 12V@2A, 6V@4A, 24V@1A etc.
- The protection diode should preferably be a schottky type, which has better response times. Something like a MUR340 is good for loads up to 3A.

